



**Department of Computer Science & Engineering**

**Course No : CSE 2106**

**Course Title : Digital Logic Design Sessional**

**Experiment No : 10**

**Experiment Name :** (a) Design a switch controlled Binary random up-down counter using J-K Flip-Flop for following sequence.  
If  $s=0$  down,  $3 \leftarrow 0 \leftarrow 5 \leftarrow 2 \leftarrow 1$   
If  $s=1$  up,  $3 \rightarrow 0 \rightarrow 5 \rightarrow 2 \rightarrow 1$   
(b) Design a 4 bit Synchronous down counter using TFF  
(c) Design a BCD Ripple Up Counter using D Flip-Flop

**Date of Submission : 26-02-22**

**Submitted to : Zarin Tasnim Shejuti & Tamanna Tabassum**

**Submitted By-**

**Group No : Group-5(A2)**

**Name : Yasir Arsalan Prince**

**Student Id : 20200101042**

**Section : A**


Experiment Name: (a) Design a Switch Controlled Binary Random Up-down Counter Using J-k Flip-Flop for the following Sequence:

If  $S=0$ , Down :  $3 \leftarrow 0 \leftarrow 5 \leftarrow 2 \leftarrow 4$

If  $S=1$ , Up :  $3 \rightarrow 0 \rightarrow 5 \rightarrow 2 \rightarrow 4$

Objective: In this experiment, we are going to design a switch controlled binary random up-down Counter using J-k flip-flop. If the Switch,  $S=0$  it will work as down counter otherwise, if the switch  $S=1$  it will work as a up counter.

State Diagram:

 

State Table:

Switch	Present State	Next State
0(down)	3	4
	0	3
	5	0
	2	5
	4	2
1(up)	3	0
	0	5
	5	2
	2	4
	4	3

Number of flip-flop: In the sequence, the maximum value is 5, so the number of flip-flops =  $\lceil \log_2 5 \rceil = 3$

Excitation Table:

Decimal	Switch	Present State			Next State			JK FF's input					
		$Q_3$	$Q_2$	$Q_1$	$Q_3'$	$Q_2'$	$Q_1'$	$J_3$	$K_3$	$J_2$	$K_2$	$J_1$	$K_1$
3	0	0	1	1	1	0	0	1	X	X	1	X	1
0	0	0	0	0	0	1	1	0	X	1	X	1	X
5	0	1	0	1	0	0	0	X	1	0	X	X	1
2	0	0	1	0	1	0	1	1	X	X	1	1	X
4	0	1	0	0	0	1	0	X	1	1	X	0	X
11	1	0	1	1	0	0	0	0	X	X	1	X	1
8	1	0	0	0	1	0	1	1	X	0	X	1	X
13	1	1	0	1	0	1	0	X	1	1	X	X	1
10	1	0	1	0	1	0	0	1	X	X	1	0	X
12	1	1	0	0	0	1	1	X	1	1	X	1	X

Function Simplification using k-map:

Here, Common don't care,  $d = \Sigma (1, 6, 7, 9, 14, 15)$

$$J_3 = \Sigma (3, 2, 8, 10)$$

$$K_3 = \Sigma (4, 5, 12, 13)$$

$$d = \Sigma (1, 4, 5, 6, 7, 9, 12, 13, 14, 15)$$

$$d = \Sigma (1, 2, 3, 6, 7, 8, 9, 10, 11, 14, 15)$$

$Q_2 Q_1$	$\bar{Q}_2 \bar{Q}_1$	$\bar{Q}_2 Q_1$	$Q_2 \bar{Q}_1$	$Q_2 Q_1$
$\bar{S} Q_3$		X	1	1
$\bar{S} \bar{Q}_3$	X	X	X	X
$S Q_3$	X	X	X	X
$S \bar{Q}_3$	1	X		1

$$J_3 = \bar{S} Q_2 + S \bar{Q}_1$$

$Q_2 Q_1$	$\bar{Q}_2 \bar{Q}_1$	$\bar{Q}_2 Q_1$	$Q_2 \bar{Q}_1$	$Q_2 Q_1$
$\bar{S} \bar{Q}_3$	X	X	X	X
$\bar{S} Q_3$	1	1	X	X
$S Q_3$	1	1	X	X
$S \bar{Q}_3$	X	X	X	X

$$K_3 = 1$$

$$\overline{Q}_2 = \Sigma(0, 4, 12, 13)$$

$$d = \Sigma(1, 2, 3, 7, 9, 6, 10, 11, 14, 15)$$

$Q_2 Q_1$	$\overline{Q}_2 \overline{Q}_1$	$\overline{Q}_2 Q_1$	$Q_2 \overline{Q}_1$	$Q_2 Q_1$
$\overline{S} Q_3$	1	X	X	X
$\overline{S} \overline{Q}_3$	1		X	X
$S Q_3$	1	1	X	X
$S \overline{Q}_3$		X	X	X

$$\overline{Q}_2 = S Q_3 + \overline{S} \overline{Q}_1$$

$$\overline{Q}_1 = \Sigma(0, 2, 8, 12)$$

$$d = \Sigma(1, 3, 5, 6, 7, 9, 11, 13, 14, 15)$$

$Q_2 Q_1$	$\overline{Q}_2 \overline{Q}_1$	$\overline{Q}_2 Q_1$	$Q_2 \overline{Q}_1$	$Q_2 Q_1$
$\overline{S} \overline{Q}_3$	1	X	X	1
$\overline{S} Q_3$		X	X	X
$S Q_3$	1	X	X	X
$S \overline{Q}_3$	1	X	X	

$$\overline{Q}_1 = \overline{S} \overline{Q}_3 + S \overline{Q}_2$$

$$K_2 = \Sigma(2, 3, 10, 11)$$

$$d = \Sigma(0, 1, 4, 5, 6, 7, 8, 9, 12, 13, 14, 15)$$

$Q_2 Q_1$	$\overline{Q}_2 \overline{Q}_1$	$\overline{Q}_2 Q_1$	$Q_2 \overline{Q}_1$	$Q_2 Q_1$
$\overline{S} \overline{Q}_3$	X	X	1	1
$\overline{S} Q_3$	X	X	X	X
$S Q_3$	X	X	X	X
$S \overline{Q}_3$	X	X	1	1


$$K_2 = 1$$

$$K_1 = \Sigma(3, 5, 11, 13)$$

$$d = \Sigma(0, 1, 2, 4, 6, 7, 8, 9, 10, 12, 14, 15)$$

$Q_2 Q_1$	$\overline{Q}_2 \overline{Q}_1$	$\overline{Q}_2 Q_1$	$Q_2 \overline{Q}_1$	$Q_2 Q_1$
$\overline{S} \overline{Q}_3$	X	X	1	X
$\overline{S} Q_3$	X	1	X	X
$S Q_3$	X	1	X	X
$S \overline{Q}_3$	X	X	1	X

$$K_1 = 1$$

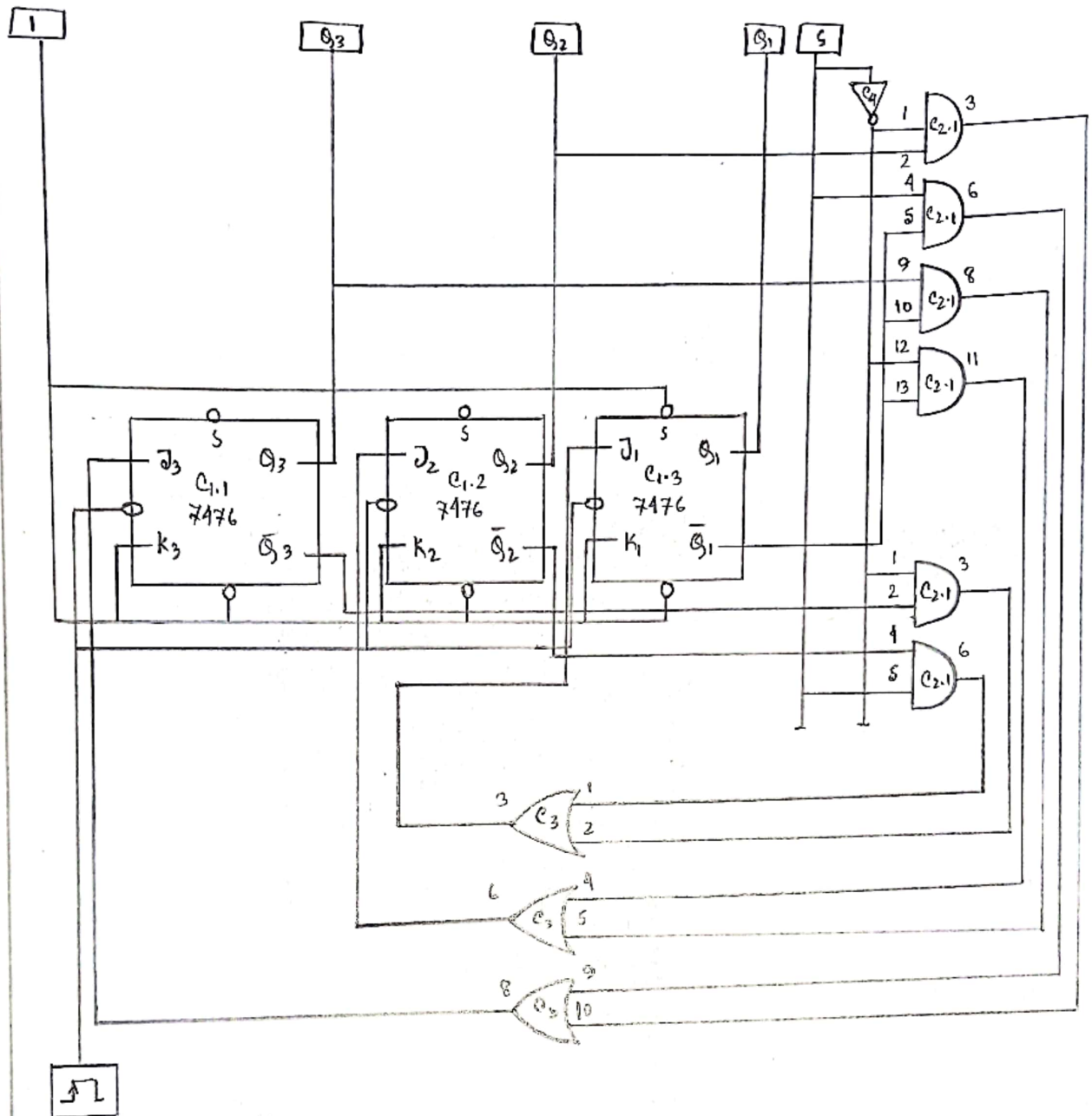Circuit Diagram:



10 Requirements;


1. JK Flip-flop (7476  $\rightarrow$  C<sub>1</sub>) - 3 pieces
2. AND (74LS08) - 2 pieces
3. OR (74LS32  $\rightarrow$  C<sub>3</sub>) - 1 piece
4. NOT (74LS04  $\rightarrow$  C<sub>4</sub>) - 1 piece

Conclusion: From this experiment, we have constructed a switch controlled binary random up-down counter using JK flip-flop. When the switch is turned off it works as down counter and when the switch is on it works as up counter.

Experiment Name: (b) Design a 4 bit Synchronous Down-Counter using T Flip-Flop.

Objective: Here, we are going to construct a circuit for 4 bit Synchronous Down Counter using T Flip-Flop. JK Flip-Flop can work as a T Flip-Flop if we input the same value in J & K. Hence both the values of J and K can either be zero or one. By using this method, we can construct a JK flip-flop IC into a T Flip-Flop IC.

State Diagram:

 

State Table:

Present State	Next State
0	15
1	0
2	1
3	2
4	3
5	4
6	5
7	6
8	7
9	8
10	9
11	10
12	11
13	12
14	13
	14

Number of Flip-Flop:

Highest Number = 15  
Number of Flip-Flop =  $\lceil \log_2 15 \rceil = 4$

Excitation Table:

Decimal	Present State				Next State				Flip Flop Input			
	$Q_4'$	$Q_3'$	$Q_2'$	$Q_1'$	$Q_4$	$Q_3$	$Q_2$	$Q_1$	$T_4$	$T_3$	$T_2$	$T_1$
0	0	0	0	0	1	1	1	1	1	1	1	1
1	0	0	0	1	0	0	0	0	0	0	0	1
2	0	0	1	0	0	0	0	1	0	0	1	1
3	0	0	1	1	0	0	1	0	0	0	0	1
4	0	1	0	0	0	0	1	1	0	1	1	1
5	0	1	0	1	0	1	0	0	0	0	0	1
6	0	1	1	0	0	1	0	1	0	0	1	1
7	0	1	1	1	0	1	1	0	0	0	0	1
8	1	0	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	0	0	0	0	0	0	1
10	1	0	1	0	1	0	0	1	0	0	1	1
11	1	0	1	1	1	0	1	0	0	0	0	1
12	1	1	0	0	1	0	1	1	0	1	1	1
13	1	1	0	1	1	1	0	0	0	0	0	1
14	1	1	1	0	1	1	0	1	0	0	1	1
15	1	1	1	1	1	1	1	0	0	0	0	1



Function Simplification using k-map:

$$T_1 = \Sigma(0, 8)$$

$Q_4 Q_3 \backslash Q_2 Q_1$	$\bar{Q}_2 \bar{Q}_1$	$\bar{Q}_2 Q_1$	$Q_2 \bar{Q}_1$	$Q_2 Q_1$
$\bar{Q}_4 \bar{Q}_3$	11			
$\bar{Q}_4 Q_3$				
$Q_4 \bar{Q}_3$				
$Q_4 Q_3$	11			

$$T_1 = \bar{Q}_3 \bar{Q}_2 \bar{Q}_1$$

$$T_3 = \Sigma(0, 4, 8, 12)$$

$Q_4 Q_3 \backslash Q_2 Q_1$	$\bar{Q}_2 \bar{Q}_1$	$\bar{Q}_2 Q_1$	$Q_2 \bar{Q}_1$	$Q_2 Q_1$
$\bar{Q}_4 \bar{Q}_3$	1			
$\bar{Q}_4 Q_3$	1			
$Q_4 \bar{Q}_3$	1			
$Q_4 Q_3$	1			

$$T_3 = \bar{Q}_2 \bar{Q}_1$$

$$T_2 = \Sigma(0, 2, 4, 6, 8, 10, 12, 14)$$

$Q_4 Q_3 \backslash Q_2 Q_1$	$\bar{Q}_2 \bar{Q}_1$	$\bar{Q}_2 Q_1$	$Q_2 \bar{Q}_1$	$Q_2 Q_1$
$\bar{Q}_4 \bar{Q}_3$	1			1
$\bar{Q}_4 Q_3$	1			1
$Q_4 \bar{Q}_3$	1			1
$Q_4 Q_3$	1			1


$$T_2 = \bar{Q}_1$$

$$T_1 = \Sigma(0, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$Q_4 Q_3 \backslash Q_2 Q_1$	$\bar{Q}_2 \bar{Q}_1$	$\bar{Q}_2 Q_1$	$Q_2 \bar{Q}_1$	$Q_2 Q_1$
$\bar{Q}_4 \bar{Q}_3$	1	1	1	1
$\bar{Q}_4 Q_3$	1	1	1	1
$Q_4 \bar{Q}_3$	1	1	1	1
$Q_4 Q_3$	1	1	1	1

$$T_1 = 1$$

### Circuit Diagram:

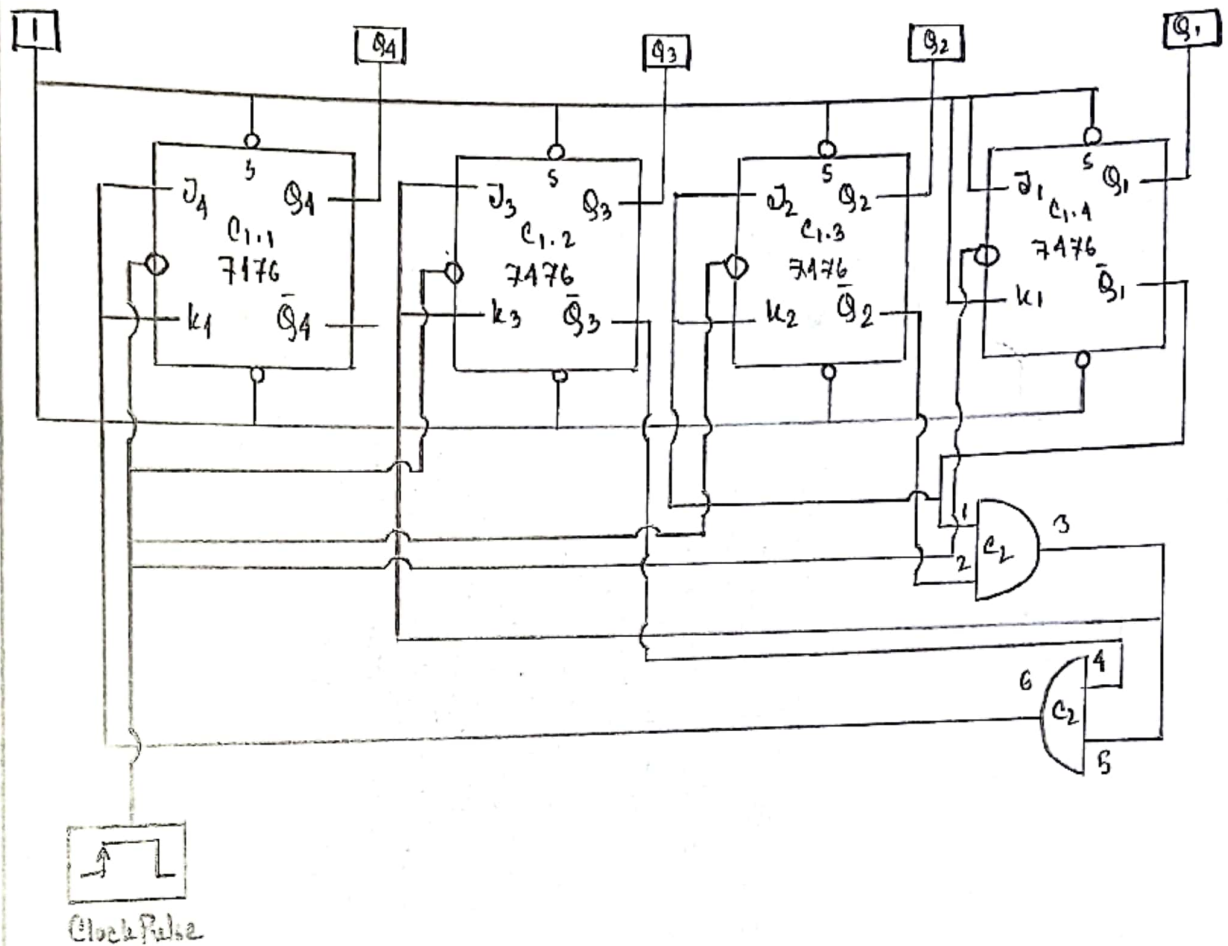

### IC Requirement:


1. JKFF (7476) → 4 pieces
2. C<sub>2</sub> → AND Gate (74LS08) → 1 piece

Conclusion: In this experiment, we have constructed a circuit for 4 bit Synchronous down counter using T Flip-Flop. Synchronous means its clock pulse never depends on the output values. We need to input position level clock value and thus the four JK Flip-Flop works at a same time for this experiment.

Experiment Name: (c) Design a BCD Ripple up counter using D flip-flop.

Objective: Our objective is to design a BCD Ripple up counter using a D flip-flop. This counter is designed to count ten digits, (0-9). It counts for every new clock input.

State Diagram:

 

State Table:


Present State	Next State
0	1
1	2
2	3
3	4
4	5
5	6
6	7
7	8
8	9
9	0

Number of Flip-flop: In the sequence, the maximum value is 9. So, the number of flip-flop =  $\lceil \log_2 9 \rceil = 4$

D-Flipflop Excitation Table:

$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

Circuit Diagram:

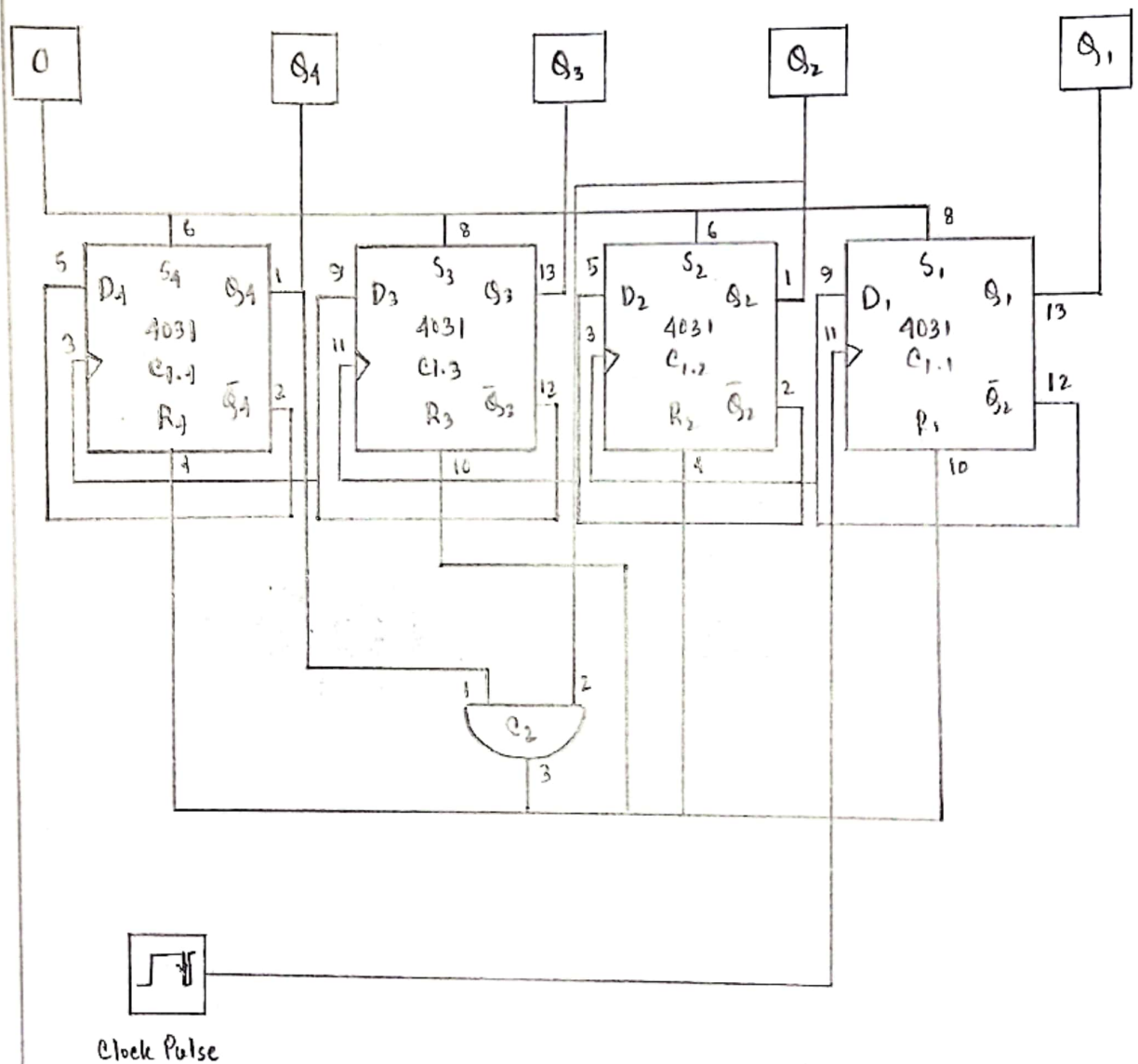

IC Requirements:

1.  $C_1 \rightarrow 4013$  (D-Flip Flop) - 4 pieces
2.  $C_2 \rightarrow 74LS08$  (AND Gate) - 1 piece

Conclusion: We have constructed a BCD ripple up counter using D-Flip Flop. Hence, the connection were given properly and required output was found.