

Department of Computer Science & Engineering

CourseNo : CSE2106

Course Title : Digital Logic Design Sessional

Experiment No : 05

Experiment Name : a) Design a switch(s) controlled Even/Odd parity checker circuit for 4 bit data
if S=0 then Even parity
if S=1 then Odd parity
b) Design a Excess-4 to BCD Converter Circuit
c) Design a switch(s) controlled 4 bit Binary to Gray & Gray to Binary code conversion circuit
if S=0 then Gray to Binary Code
if S=1 then Binary to Gray Code

Date of Submission : 10 Jan 2022

Submitted to: Ms. Qamrun Nahar Eity & Tamanna Tabassum

Submitted By-

Group No : 05(A2)

Name : Yasir Arafah Prince

Id : 20200104042

Section : A

Experiment Name: Design a switch(s) controlled even/odd Parity checker circuit for 4-bit Data. If $s=0$, then Even parity. If $s=1$ then odd parity.

Objective: To make a number of 1's either odd or even, a extra bit is included with a binary message which is called parity bit. The receiver checks even/odd parity as a result of the calculation of the number of 1's in the message bit. If the number is even, F gets the value 1 & if the number is odd, the F gets 0. At odd parity, F gets 1 when the number of 1's is odd and 0 when the number of 1's is even. Our objective is to check a switch controlled even/odd parity circuit for 4 bit.

Truth Table:

Input					Output
S	A	B	C	D	F
0	0	0	0	0	1
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	1
0	1	1	0	1	0
0	1	1	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	0	1	1
1	0	0	1	0	1
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	1
1	1	1	1	1	0

Here $F_7 = \Sigma (0, 3, 5, 6, 9, 10, 12, 15, 17, 18, 20, 23, 24, 27, 29, 30)$

k-map:

$\begin{matrix} \text{SA} \\ \text{BCD} \end{matrix}$	$\bar{B}\bar{C}\bar{D}$	$\bar{B}\bar{C}D$	$\bar{B}CD$	$\bar{B}C\bar{D}$	$B\bar{C}\bar{D}$	$B\bar{C}D$	$BC\bar{D}$	BCD
$\bar{S}\bar{A}$	1		1		1		1	
$\bar{S}A$		1		1		1		1
SA	1		1		1		1	
$S\bar{A}$		1		1		1		1

$$F = \bar{S}\bar{A}\bar{B}\bar{C}\bar{D} + \bar{S}\bar{A}\bar{B}C\bar{D} + \bar{S}\bar{A}B\bar{C}\bar{D} + \bar{S}\bar{A}B\bar{C}D + \bar{S}A\bar{B}\bar{C}\bar{D} + \bar{S}A\bar{B}C\bar{D} + \bar{S}AB\bar{C}\bar{D} + \bar{S}AB\bar{C}D + SA\bar{B}\bar{C}\bar{D} + SA\bar{B}C\bar{D} + SAB\bar{C}\bar{D} + SAB\bar{C}D + S\bar{A}\bar{B}\bar{C}\bar{D} + S\bar{A}\bar{B}C\bar{D} + S\bar{A}B\bar{C}\bar{D} + S\bar{A}B\bar{C}D$$

$$= \bar{S}\bar{A}\bar{B}(\bar{C}\bar{D} + C\bar{D}) + \bar{S}\bar{A}B(\bar{C}\bar{D} + C\bar{D}) + \bar{S}A\bar{B}(\bar{C}D + C\bar{D}) + \bar{S}AB(\bar{C}D + C\bar{D}) + SA\bar{B}(\bar{C}\bar{D} + C\bar{D}) + SAB(\bar{C}\bar{D} + C\bar{D}) + S\bar{A}\bar{B}(\bar{C}D + C\bar{D}) + S\bar{A}B(\bar{C}D + C\bar{D})$$

[Distributive Law]

$$= \bar{S}\bar{A}\bar{B}(\overline{C \oplus D}) + \bar{S}\bar{A}B(\overline{C \oplus D}) + \bar{S}A\bar{B}(\overline{C \oplus D}) + \bar{S}AB(\overline{C \oplus D}) + SA\bar{B}(\overline{C \oplus D}) + SAB(\overline{C \oplus D}) + S\bar{A}\bar{B}(\overline{C \oplus D}) + S\bar{A}B(\overline{C \oplus D})$$

[Definition of X-OR, X-NOR]

$$= \bar{S}\bar{A}\bar{B}(\overline{C \oplus D}) + \bar{S}A\bar{B}(\overline{C \oplus D}) + \bar{S}\bar{A}B(\overline{C \oplus D}) + \bar{S}AB(\overline{C \oplus D}) + SA\bar{B}(\overline{C \oplus D}) + SAB(\overline{C \oplus D}) + S\bar{A}\bar{B}(\overline{C \oplus D}) + S\bar{A}B(\overline{C \oplus D})$$

[Commutative Law]

$$= \bar{S}(\bar{A}\bar{B} + AB)(\overline{C \oplus D}) + \bar{S}(\bar{A}B + A\bar{B})(\overline{C \oplus D}) + S(A\bar{B} + \bar{A}B)(\overline{C \oplus D}) + S(AB + \bar{A}\bar{B})(\overline{C \oplus D})$$

[Distributive Law]

$$= \bar{S}(\overline{A \oplus B})(\overline{C \oplus D}) + \bar{S}(A \oplus B)(\overline{C \oplus D}) + S(\overline{A \oplus B})(\overline{C \oplus D}) + S(A \oplus B)(\overline{C \oplus D})$$

[Distributive Law]

$$= \bar{S}(\overline{(A \oplus B) \oplus (C \oplus D)}) + S((A \oplus B) \oplus (C \oplus D))$$


[Definition of X-OR, X-NOR]

$$= S \oplus ((A \oplus B) \oplus (C \oplus D))$$

[Definition of X-NOR]

Using k-map the simplified expression is, $F = S \oplus ((A \oplus B) \oplus (C \oplus D))$

Circuit Diagram:

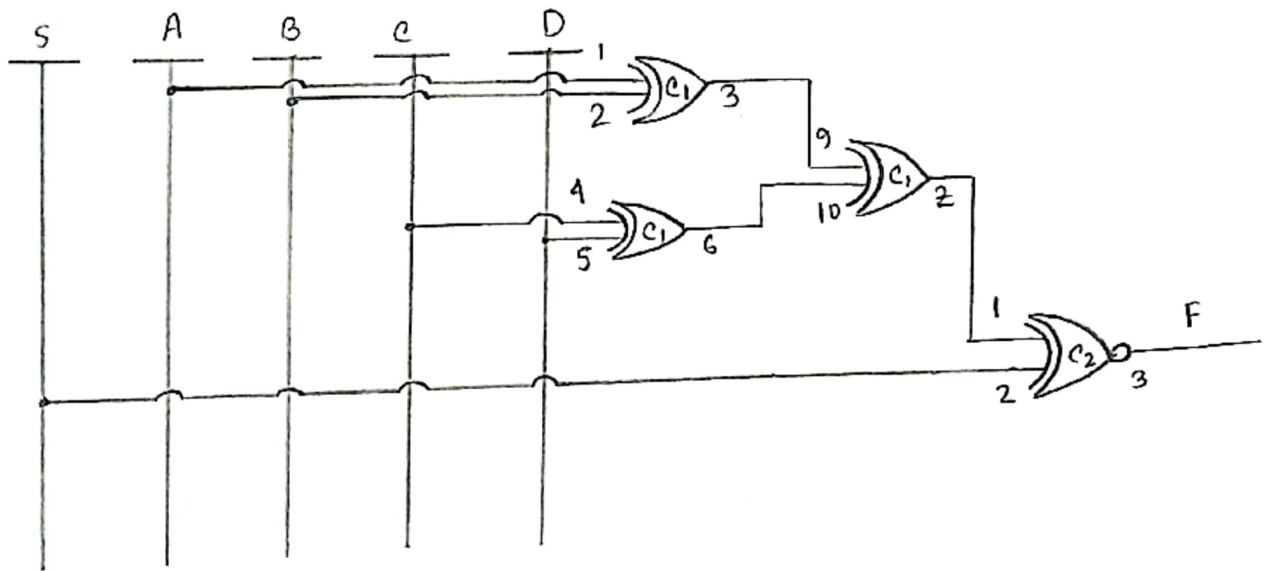

IC Requirements:

1. C_1 - 74LS86 (X-OR Gate) - 1 piece
2. C_2 - 74LS266 (X-NOR Gate) - 1 piece

Conclusion: In this experiment, we have learnt that it is a 4-bit switch controlled odd and even parity and we can check for both odd and even parity. From the truth table and the k-map we have obtained the simplified expression which we implemented in the circuit with proper IC requirements.

Experiment Name: Design a excess-4 to BCD converter circuit

Objective: BCD is the abbreviation of Binary Coded Decimal and Excess-4 codes are unweighted codes which are obtained by adding 4 to each decimal digit and can be represented by binary representation. In this experiment, we are going to design a circuit of Excess-4 to BCD and using k-map to obtain simplified expression.

Truth Table:

Decimal Value	Excess-4				BCD			
	A	B	C	D	w	x	y	z
0	0	0	0	0	x	x	x	x
1	0	0	0	1	x	x	x	x
2	0	0	1	0	x	x	x	x
3	0	0	1	1	x	x	x	x
4	0	1	0	0	0	0	0	0
5	0	1	0	1	0	0	0	1
6	0	1	1	0	0	0	1	0
7	0	1	1	1	0	0	1	1
8	1	0	0	0	0	1	0	0
9	1	0	0	1	0	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	0	1	1	1
12	1	1	0	0	1	0	0	0
13	1	1	0	1	1	0	0	1
14	1	1	1	0	x	x	x	x
15	1	1	1	1	x	x	x	x

Function Evaluation:

For $w = \Sigma(12,13)$ $d = \Sigma(0,1,2,3,14,15)$

k-map:

$AB \backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	x	x	x	x
$\bar{A}B$				
AB	1	1	x	x
$A\bar{B}$				

Using k-map, the simplified function is $w = AB$

For x , $x = \Sigma(8,9,10,11)$ $d = \Sigma(0,1,2,3,14,15)$

k-map:

$AB \backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	x	x	x	x
$\bar{A}B$				
AB			x	x
$A\bar{B}$	1	1	1	1

Using k-map, the simplified function is $x = \bar{B}$

For y , $y = \Sigma(6,7,10,11)$ $d = \Sigma(0,1,2,3,14,15)$

k-map:

$AB \backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	x	x	x	x
$\bar{A}B$			1	1
AB			x	x
$A\bar{B}$			1	1

Using k-map, the simplified function is $y = C$


For $z, z = \Sigma(5, 7, 9, 11, 13) \quad d = \Sigma(0, 1, 2, 3, 14, 15)$

k-map:

$AB \backslash CD$	$\bar{c}\bar{d}$	$\bar{c}d$	cd	$c\bar{d}$
$\bar{A}\bar{B}$	x	x	x	x
$\bar{A}B$		1	1	
AB		1	x	x
$A\bar{B}$		1	1	

Using k-map the simplified function is, $z = D$

Circuit Diagram:

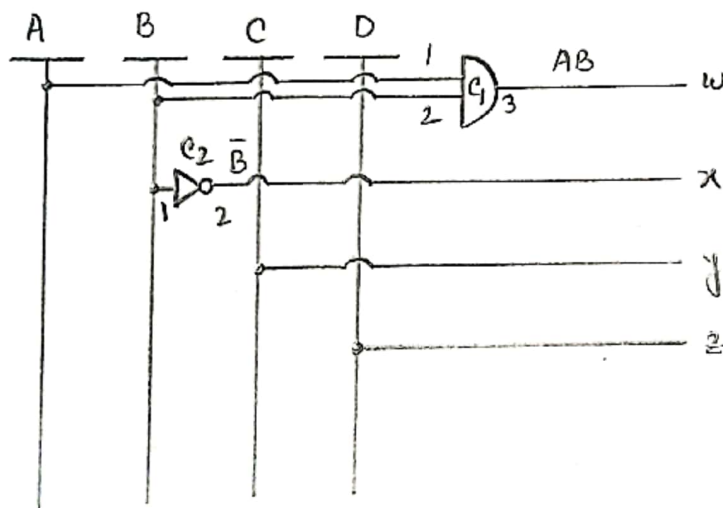

IC Requirements:

- i) $IC_1 \rightarrow 74LS08$ (AND Gate) - 1 piece
- ii) $IC_2 \rightarrow 74LS04$ (NOT Gate) - 1 piece

Conclusion: In this experiment, we have learned the conversion of Excess-4 to BCD where (0-3) and (14-15) were don't cares. From the truth table and k-map we have got the minimized expression and implemented it on the circuit with proper IC requirements.

Experiment Name: Design a switch controlled 4-bit binary to Gray and Gray to binary code conversion circuit.

If $s=0$ then Gray to Binary Code

If $s=1$ then Binary to Gray Code

Objective: Binary code is a group of binary bits which are used to store, represent and transmit data is called binary code. On the other hand, Gray code is a non-weighted code. The successive gray code differ in one bit positions. The objective is to design a switch controlled binary to Gray and Gray to binary converter.

Hence, $w = \Sigma (8, 9, 10, 11, 12, 13, 14, 15, 24, 25, 26, 27, 28, 29, 30, 31)$

k-map:

SA \ BCD	$\bar{B}\bar{C}\bar{D}$	$\bar{B}\bar{C}D$	$\bar{B}C\bar{D}$	$\bar{B}CD$	$BC\bar{D}$	BCD	$B\bar{C}D$	$B\bar{C}\bar{D}$
$\bar{S}\bar{A}$	0	0	0	0	0	0	0	0
$\bar{S}A$	1	1	1	1	1	1	1	1
SA	1	1	1	1	1	1	1	1
SA	0	0	0	0	0	0	0	0

Using k-map, simplified expression is, $w = A$

Hence, $x = \Sigma (1, 5, 6, 7, 8, 9, 10, 11, 20, 21, 22, 23, 24, 25, 26, 27)$

SA \ BCD	$\bar{B}\bar{C}\bar{D}$	$\bar{B}\bar{C}D$	$\bar{B}C\bar{D}$	$\bar{B}CD$	$BC\bar{D}$	BCD	$B\bar{C}D$	$B\bar{C}\bar{D}$
$\bar{S}\bar{A}$	0	0	0	0	1	1	1	1
$\bar{S}A$	1	1	1	1	0	0	0	0
SA	1	1	1	1	0	0	0	0
SA	0	0	0	0	1	1	1	1

Using k-map, the simplified expression is, $x = A\bar{B} + \bar{A}B = A \oplus B$

Hence, $y = \Sigma (2, 3, 4, 5, 8, 9, 14, 15, 18, 19, 20, 21, 26, 27, 28, 29)$

SA \ BCD	$\bar{B}\bar{C}\bar{D}$	$\bar{B}\bar{C}D$	$\bar{B}C\bar{D}$	$\bar{B}CD$	$BC\bar{D}$	BCD	$B\bar{C}D$	$B\bar{C}\bar{D}$
$\bar{S}\bar{A}$	0	0	1	1	0	0	1	1
$\bar{S}A$	1	1	0	0	1	1	0	0
SA	0	0	1	1	0	0	1	1
SA	0	0	1	1	0	0	1	1

$$y = \bar{A}\bar{B}C + \bar{S}\bar{B}C + \bar{S}ABC + \bar{A}B\bar{C} + SB\bar{C} + \bar{S}A\bar{B}\bar{C}$$

$$= \bar{S}ABC + \bar{S}A\bar{B}\bar{C} + \bar{S}\bar{B}C + SB\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} \quad [\text{Commutative Law}]$$

$$\begin{aligned}
&= \bar{s}A(B\bar{c} + \bar{B}c) + s(\bar{B}c + B\bar{c}) + \bar{A}(B\bar{c} + \bar{B}c) \quad [\text{Distributive Law}] \\
&= \bar{s}A(\overline{B \oplus c}) + s(B \oplus c) + \bar{A}(B \oplus c) \quad [\text{Definition of X-OR and X-NOR}] \\
&= \bar{s}A(\overline{B \oplus c}) + (s + \bar{A})(B \oplus c) \quad [\text{Distributive Law}] \\
&= \bar{s}A(\overline{B \oplus c}) + (\overline{s + \bar{A}})(B \oplus c) \quad [\text{Double Negation}] \\
&= \bar{s}A(\overline{B \oplus c}) + \overline{s \cdot \bar{A}}(B \oplus c) \quad [\text{De Morgan's Law}] \\
&= \bar{s}A(\overline{B \oplus c}) + \overline{s \cdot A}(B \oplus c) \quad [\text{Double Negation}] \\
&= \bar{s}A \oplus B \oplus c \quad [\text{Definition of X-OR}] \\
\therefore y &= \bar{s}A \oplus B \oplus c \quad [\text{using k-map}]
\end{aligned}$$

$$\text{Now, } z = \Sigma(1, 2, 4, 7, 8, 11, 13, 14, 17, 18, 21, 22, 25, 26, 29, 30)$$

$\begin{matrix} BCD \\ SA \end{matrix}$	$\bar{B}\bar{c}\bar{D}$	$\bar{B}\bar{c}D$	$\bar{B}c\bar{D}$	$\bar{B}cD$	$B\bar{c}\bar{D}$	$B\bar{c}D$	$Bc\bar{D}$	BcD
$\bar{s}\bar{A}$	0	1	0	1	0	1	0	1
$\bar{s}A$	1	0	1	0	1	0	1	0
sA	0	1	0	1	1	0	1	0
$s\bar{A}$	0	1	0	1	1	0	1	0

$$\begin{aligned}
z &= s\bar{c}D + sc\bar{D} + \bar{A}\bar{B}\bar{c}D + \bar{A}\bar{B}c\bar{D} + AB\bar{c}D + ABc\bar{D} + \bar{s}\bar{A}BCD + \bar{s}\bar{A}B\bar{c}D + \\
&\quad \bar{s}A\bar{B}\bar{c}\bar{D} + \bar{s}A\bar{B}cD
\end{aligned}$$

$$\begin{aligned}
&= s(\bar{c}D + c\bar{D}) + \bar{A}\bar{B}(\bar{c}D + c\bar{D}) + AB(\bar{c}D + c\bar{D}) + \bar{s}\bar{A}B(cD + \bar{c}\bar{D}) + \\
&\quad \bar{s}A\bar{B}(\bar{c}\bar{D} + cD) \quad [\text{Distributive Law}]
\end{aligned}$$

$$\begin{aligned}
&= s(c \oplus D) + \bar{A}\bar{B}(c \oplus D) + AB(c \oplus D) + \bar{s}\bar{A}B(\overline{c \oplus D}) + \bar{s}A\bar{B}(\overline{c \oplus D}) \\
&\quad [\text{Definition of X-OR and X-NOR}]
\end{aligned}$$

$$= (S + \bar{A}\bar{B} + AB)(C \oplus D) + \bar{S}(\bar{A}B + A\bar{B})(\overline{C \oplus D}) \quad [\text{Distributive Law}]$$

$$= (S + \overline{A \oplus B})(C \oplus D) + \bar{S}(A \oplus B)(\overline{C \oplus D}) \quad \left[\begin{array}{l} \text{Definition of X-OR and} \\ \text{X-NOR} \end{array} \right]$$

$$= (\overline{\overline{S + \overline{A \oplus B}}})(C \oplus D) + \bar{S}(A \oplus B)(\overline{C \oplus D}) \quad [\text{Complement Law}]$$

$$= \bar{S} \cdot (\overline{\overline{A \oplus B}})(C \oplus D) + \bar{S}(A \oplus B)(\overline{C \oplus D}) \quad [\text{De-Morgan's Law}]$$

$$= \bar{S} \cdot (A \oplus B)(C \oplus D) + \bar{S}(A \oplus B)(\overline{C \oplus D}) \quad [\text{Double Negation}]$$

$$= \bar{S}(A \oplus B) \oplus (C \oplus D) \quad [\text{Definition of X-OR}]$$

$$Z = \bar{S}(A \oplus B) \oplus (C \oplus D)$$


Circuit Diagram:

$$w = A$$

$$x = A \oplus B$$

$$y = (\bar{S}A) \oplus B \oplus C$$
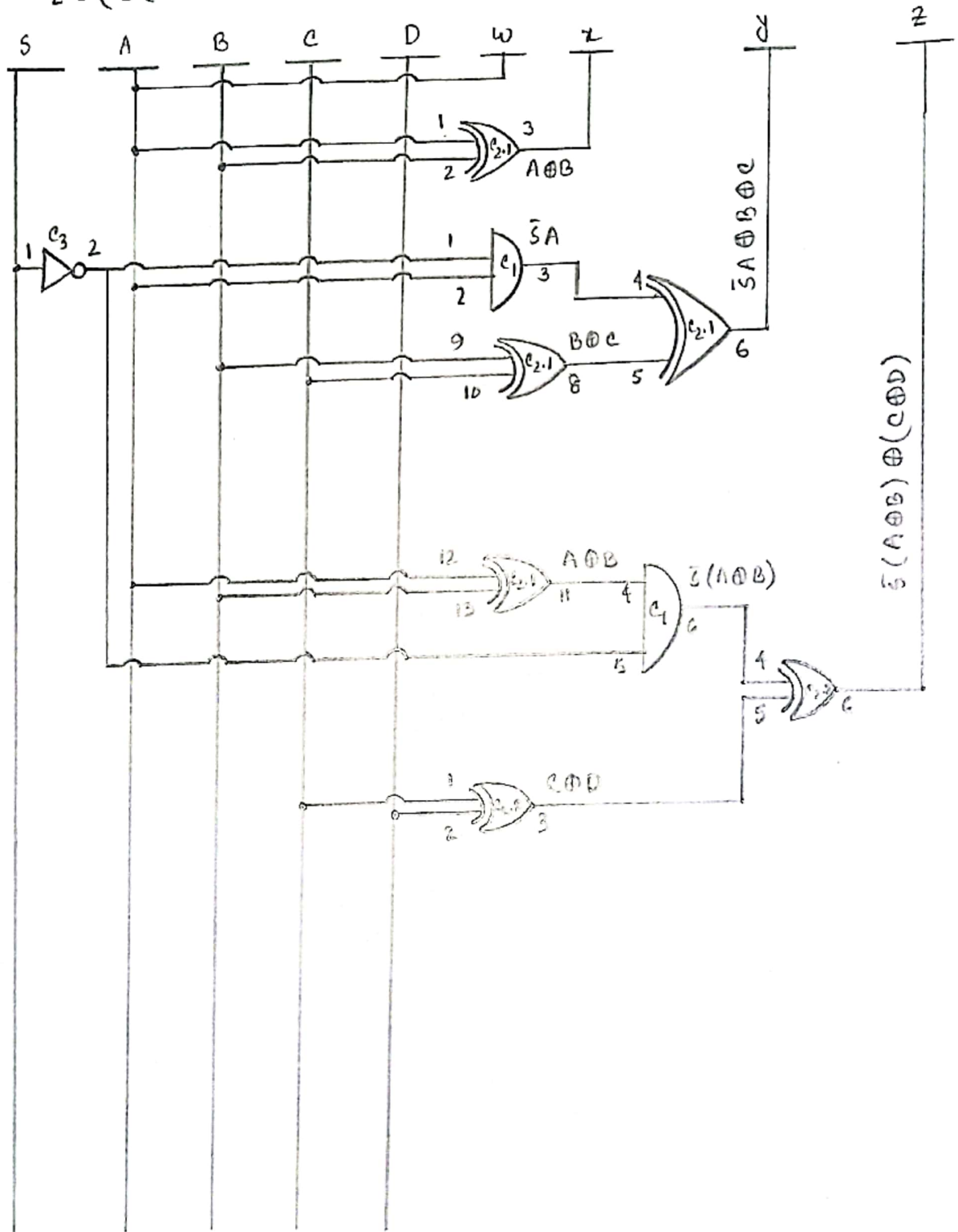
$$z = (\bar{S}(A \oplus B)) \oplus (C \oplus D)$$



IC Requirements:

1. $C_1 \rightarrow 74LS08$ (AND Gate) - 1 piece
2. $C_2 \rightarrow 74LS86$ (XOR Gate) - 2 pieces
3. $C_3 \rightarrow 74LS04$ (NOT Gate) - 1 piece

Conclusion: From the experiment, we have learnt that it is a 4-bit switch controlled Binary to Gray and Gray to Binary code converter. if $s = 0$, then (0-15) will be converted into gray to binary, when $s = 1$ then (16-31) will be converted into binary to gray. And implemented the minimized expressions in the circuit.